

## Multiple Choice:

### Version A


- 1) xii.
- 2) ii.
- 3) v.
- 4) i.

### Version B

- 1) vi.
- 2) x.
- 3) vi.
- 4) ii.

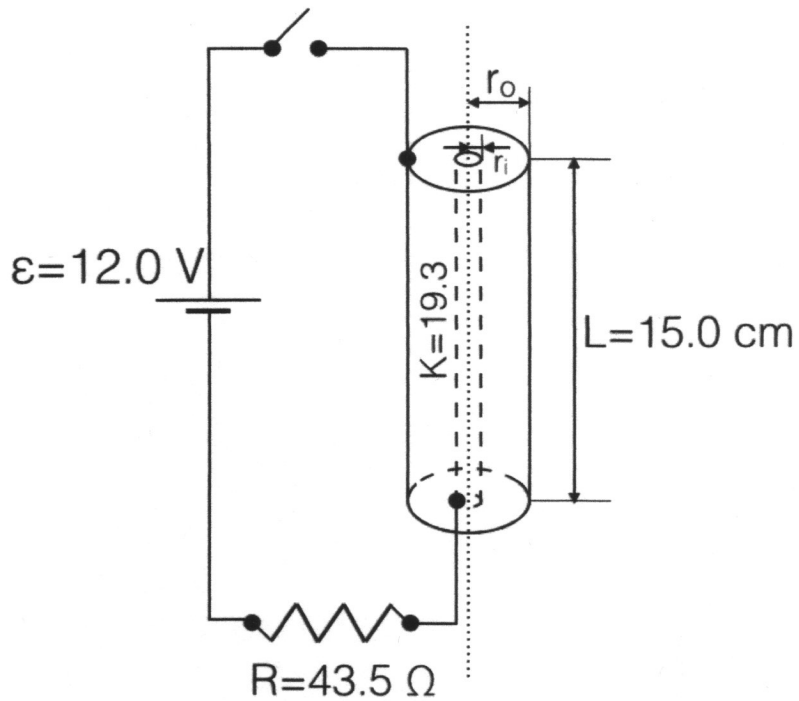**Problem II. (20 points)**

A cylindrical capacitor of length  $L = 15.0$  cm with inner radius of  $r_i = 0.20$  cm and outer radius of  $r_o = 1.0$  cm has an insulating material between the plates with a dielectric constant of  $K=19.3$ . It is connected to an emf  $\mathcal{E}=12.0$  V that has negligible internal resistance through a resistor  $R=43.5 \Omega$  and a switch (as shown in the figure). The capacitor is initially uncharged and the switch is open (OFF position).



- Find capacitance of the capacitor.
- How much time does it take to charge this capacitor to 90% of its final charge after the switch is closed (ON position).

a)

$$C = \frac{Q}{V} \quad - \text{definition of a capacitance}$$

$$Q = \lambda L \quad - \lambda \text{ is linear charge density; } \lambda = \frac{Q}{L}$$

Use Gauss's law to find field due to linear charge dist.:

$$\oint \vec{E} \cdot d\vec{A} = \frac{q}{\epsilon} \quad ; \quad \epsilon = K \epsilon_0$$

inside cap.:

$$r_o E 2\pi r l = \frac{\lambda l}{\epsilon_{r_i}} \quad ; \quad \text{if } r < r_o \quad E = \frac{1}{2\pi \epsilon} \frac{\lambda}{r}$$

$$V_o - V_i = - \int_{r_i}^{r_o} \vec{E} \cdot d\vec{r} = - \frac{1}{2\pi \epsilon} \lambda \int_{r_i}^{r_o} \frac{dr}{r} = - \frac{\lambda}{2\pi \epsilon} \ln\left(\frac{r_o}{r_i}\right)$$

$$C = \frac{Q}{\frac{Q}{2\pi \epsilon L} \ln\left(\frac{r_o}{r_i}\right)} = 2\pi \epsilon L \frac{1}{\ln\left(\frac{r_o}{r_i}\right)} = 2\pi K \epsilon_0 L \frac{1}{\ln\left(\frac{r_o}{r_i}\right)}$$

Ver. A

$$C = 100. \text{ pF} = 0.10 \text{ nF}$$

Ver. B

$$C = \frac{227}{983} \text{ pF} = 0.23 \text{ nF} \quad 3$$

b) charging of a capacitor.

$$Q(t) = Q_f (1 - e^{-\frac{t}{RC}})$$

90% of the final charge  $\frac{Q'}{Q_f} = 0.9$

$$\frac{Q'}{Q_f} = 1 - e^{-\frac{t}{RC}}$$

$$\ln e^{-\frac{t}{RC}} = \ln \left(1 - \frac{Q'}{Q_f}\right) \Rightarrow -\frac{t}{RC} = \ln \left(1 - \frac{Q'}{Q_f}\right)$$

$$t = -RC \ln \left(1 - \frac{Q'}{Q_f}\right)$$

$$t = -RC \ln(0.1)$$

Ver. A


$$t = 10.0 \text{ ns}$$

Ver. B

$$t = \overset{49.8}{\cancel{50.4}} \text{ ns}$$

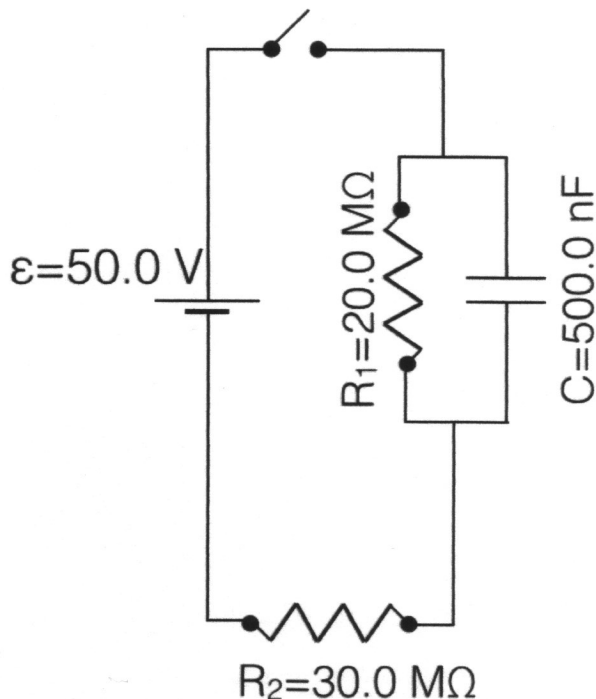**Problem III. (20 points)**

A circuit that consists of a switch, a source of emf  $\mathcal{E}=50.0$  V with negligible internal resistance, resistors  $R_1=20.0$  M $\Omega$  and  $R_2=30.0$  M $\Omega$ , and a capacitor  $C=500.0$  nF is shown in the figure.



- a) Find power dissipating in the resistor  $R_1$  after the switch has been closed for a **very long time** (consider infinite time).  
 b) After the switch has been closed for a **very long time** it is opened. Find charge on the capacitor plates **5.00** seconds after the switch was opened (OFF position).

a) After the cap. is fully charged

$$\mathcal{E} = I(R_1 + R_2) ; I = \frac{\mathcal{E}}{R_1 + R_2}$$

$$P_{R_1} = I^2 R_1 = \frac{\mathcal{E}^2}{(R_1 + R_2)^2} R_1$$

Ver. A

$$P_{R_1} = \frac{50.0^2}{(20.0 + 30.0)^2 \cdot 10^6} \cdot 20.0 = 200 \mu\text{W}$$

Ver. B

$$P_{R_1} = \frac{100.0^2}{(80.0 + 20.0)^2 \cdot 10^6} \cdot 80.0 = 80.0 \mu\text{W}$$

c) Find charge on the cap. before the switch is opened:  $Q_i = C \cdot V ; V = I R_1 = \frac{\mathcal{E}}{R_1 + R_2} \cdot R_1$

$$Q_i = \frac{\mathcal{E} \cdot C \cdot R_1}{R_1 + R_2}$$

discharge through  $R_1$

$$Q(t) = \frac{\mathcal{E} C R_1}{R_1 + R_2} e^{-\frac{t}{R_1 C}}$$


$$Q(t) = Q_i \cdot e^{-\frac{t}{R_1 C}}$$

Ver. A  $Q(t=5s) = 6.07 \mu\text{C}$  <sup>4</sup>

Ver. B  $Q(t=5s) = 3.33 \mu\text{C}$

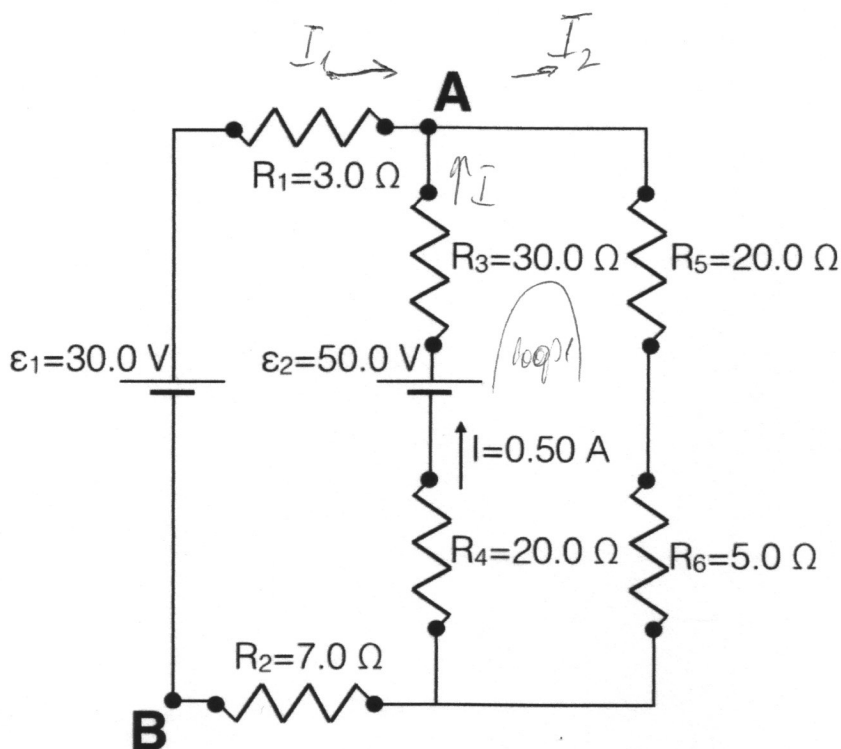**Problem IV. (20 points)**

The circuit is shown in the figure below. All emfs have negligible internal resistances. Current through the second emf  $\mathcal{E}_2$  is 0.50 A. Find potential difference between points **A** and **B** ( $V_A - V_B$ ).



Apply Kirchhoff's rules:

junction A: 
$$\underline{I}_2 = \underline{I}_1 + \underline{I}$$

loop 1: 
$$\mathcal{E}_2 - \underline{I}R_3 - \underline{I}_2R_5 - \underline{I}_2R_6 - \underline{I}R_4 = 0$$

$$\underline{I}_2 = \frac{1}{R_5 + R_6} (\mathcal{E}_2 - \underline{I}(R_3 + R_4))$$

$$\underline{I}_2 = \frac{1}{25.0} (50.0 - 0.50(50.0)) = 1.00\text{ A}$$

$$\underline{I}_1 = \underline{I}_2 - \underline{I} = 0.5\text{ A}$$

ver. A

$$V_A - V_B = \mathcal{E}_1 - \underline{I}_1 R_1 = 30.0 - 0.5 \cdot 3.0 = +28.5\text{ V}$$


ver. B

$$V_A - V_B = \mathcal{E}_1 - \underline{I}_1 R_2 = 30.0 - 0.5 \cdot 7.0 = +26.5\text{ V}$$

Ver. A

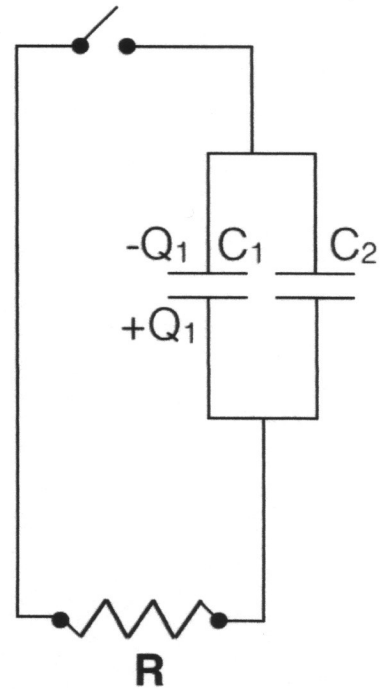**Problem V. (20 points)**

A switch, two capacitors (capacitances  $C_1$  and  $C_2$  are known) and a resistor  $R$  are connected as shown in the figure. The capacitors are charged and it is known that the  $C_1$  has charge  $Q_1$  on the plates when the switch is open. Find **total** energy dissipated in the resistor  $R$  after the switch is closed (assume that the switch remains closed for a very long time, sufficient for complete discharge of the capacitors).



Total energy stored

$$U_{\text{tot}} = \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} CV^2$$

$$V = \frac{Q_1}{C_1} \quad \text{— when the switch is open}$$

$$U_{\text{tot}} = \frac{1}{2} (C_1 + C_2) \cdot V = \frac{1}{2} (C_1 + C_2) \frac{Q_1^2}{C_1^2}$$


This energy will be dissipated in the resistor  $R$  when the switch is closed

$$E_{\text{dis}} = \frac{1}{2} (C_1 + C_2) \frac{Q_1^2}{C_1^2}$$

Ver. B

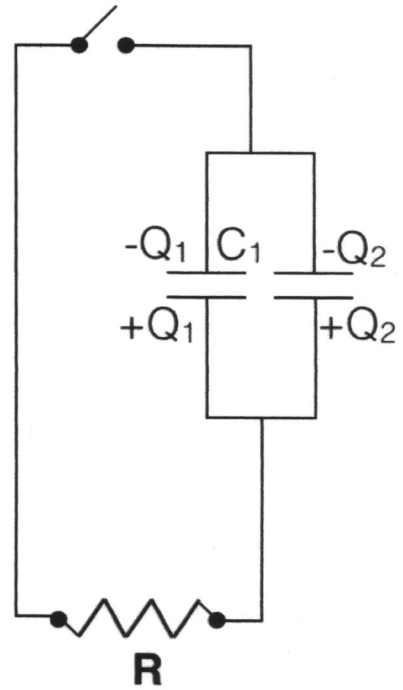**Problem V. (20 points)**

A switch, two capacitors and a resistor  $R$  are connected as shown in the figure. Capacitance  $C_1$  of the first capacitor is known but capacitance of the second one is **NOT** known. However, it is known that charge on the plates of the two capacitors is  $Q_1$  and  $Q_2$  when the switch is open. Find **total** energy dissipated in the resistor  $R$  after the switch is closed (assume that the switch remains closed for a very long time, sufficient for complete discharge of the capacitors).



Total energy stored

$$U_{\text{tot}} = \frac{1}{2} \frac{Q_1^2}{C_1} + \frac{1}{2} \frac{Q_2^2}{C_2}$$

$$V = \frac{Q_1}{C_1}; \quad V = \frac{Q_2}{C_2}; \quad C_2 = \frac{Q_2}{V} = \frac{Q_2}{Q_1} C_1$$

$$U_{\text{tot}} = \frac{1}{2} \frac{Q_1^2}{C_1} + \frac{1}{2} \frac{Q_2^2}{\frac{Q_2}{Q_1} C_1} = \frac{1}{2} \frac{Q_1^2}{C_1} + \frac{1}{2} \frac{Q_2 Q_1}{C_1}$$

This energy will be dissipated in the resistor  $R$  when the switch is closed

$$E_{\text{dis}} = \frac{1}{2} \frac{Q_1^2}{C_1} + \frac{1}{2} \frac{Q_2 Q_1}{C_1} = \frac{1}{2} \frac{Q_1}{C_1} (Q_1 + Q_2)$$