

Chapter 24 - Capacitance and Dielectrics

Physics 207

$$1. \frac{1}{C} = \frac{1}{C_{ab}} + \frac{1}{C_{bc}}$$

where $C_{ab} = 4\pi\epsilon_0 \frac{ab}{b-a}$

and $C_{bc} = 4\pi\epsilon_0 \frac{(b+t)c}{c-b-t}$

$$2. \text{ a) } C_{eff} = \frac{(\alpha+1)\epsilon_0 x^2}{2d}$$

$$2. \text{ b) } U = \frac{(\alpha+1)\epsilon_0 x^2}{4d} V^2$$

$$2. \text{ c) } U = \frac{\epsilon_0 x^2}{2d} V^2$$

$$3. \text{ a) } C_{eff} = \frac{\epsilon_0 x^2}{d-a}$$

$$3. \text{ b) } C_{eff} = \frac{\kappa\epsilon_0 x^2}{\kappa(d-a) + a}$$

3. c) No change

$$4. \text{ a) } Q_1 = C_1 V$$

$$Q_2 = C_2 V$$

$$4. \text{ b) } Q_1 = \frac{C_1 - C_2}{C_1 + C_2} C_1 V$$

$$Q_2 = \frac{C_1 - C_2}{C_1 + C_2} C_2 V$$

$$5. \text{ a) } C_{eff} = \frac{1}{3} C_1$$

$$5. \text{ b) } Q_{top} = Q_{bot} = \frac{1}{3} C_1 V_0$$

$$Q_{right} = \frac{2}{9} C_1 V_0$$

$$5. \text{ c) } V_{cd} = \frac{1}{9} V_0$$

$$6. \text{ } C_{eff} = (\sqrt{3} - 1) \frac{C}{2}$$

$$7. \text{ } C_{eff} = 96 \mu\text{F}$$