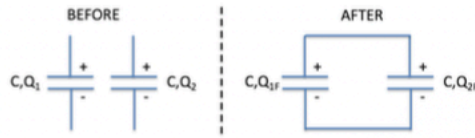


1)

[8 pts.] Two separate capacitors of the same capacitance C are initially charged to $Q_1 = 2 \mu\text{C}$ and $Q_2 = 8 \mu\text{C}$. Then their positive plates are connected to each other and their negative plates are connected to each other. The final charges Q_{1f} and Q_{2f} become :



4 μC and 6 μC

5 μC and 5 μC

4 μC and 4 μC

3 μC and 7 μC

2 μC and 4 μC

3 μC and 3 μC

$\left\{ \begin{array}{l} \text{total charge} = Q_1 + Q_2 = 8 + 2 \mu\text{C} = 10 \mu\text{C} \\ \text{since } \Delta V \text{ equal \& } C \text{ equal, final} \\ \text{charges also equal, } Q_1 = Q_2 = 5 \mu\text{C} \end{array} \right.$

2)

[8 pts.] A parallel-plate capacitor is held at a fixed voltage. If the separation of its plates is doubled, the electric energy stored in the capacitor is :

1/4 of the original

1/2 of the original

unchanged

doubled

quadrupled

$$U = \frac{1}{2} C (\Delta V)^2, \quad C = \frac{\epsilon_0 A}{d}$$

$C \rightarrow 1/2$ original with ΔV constant.

3)

[8 pts.] A charged air-filled capacitor is disconnected from the battery. A sheet of dielectric with $\kappa=3$ is inserted completely filling the volume between its plates. As a result, the electric energy stored in the capacitor is :

1/9 of the original

1/3 of the original

unchanged

tripled


here $Q = \text{const}$, so use $U = \frac{1}{2} \frac{Q^2}{C}$

$$C = \frac{\epsilon_0 A}{d} \Rightarrow \frac{\kappa \epsilon_0 A}{d} \quad (\kappa = 3 \text{ larger})$$

so U is 3x smaller

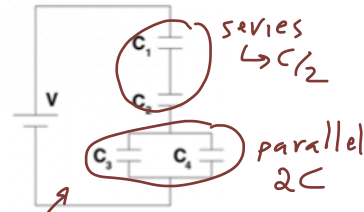4)

[10 pts.] Consider the circuit shown with voltage V and 4 capacitors with equal capacitance C . Calculate the total capacitance and the final charge on capacitor 2.



$C_{tot} = 0.25 C, Q_2 = 0.5 CV$

$C_{tot} = 0.4 C, Q_2 = 0.8 CV$

$C_{tot} = 1 C, Q_2 = 2 CV$

$C_{tot} = 0.25 C, Q_2 = 0.25 CV$

$C_{tot} = 0.4 C, Q_2 = 0.4 CV$

$C_{tot} = 1 C, Q_2 = 1 CV$

$\frac{C}{2} \{ 2C \text{ in series, } C_{eff} = \frac{(2C)(C/2)}{2.5C}$

$C_{eff} = \frac{2}{5} C$

C_2 in series \rightarrow same Q as on entire network,

$Q = C_{eff} \Delta V = \frac{2}{5} CV$

5)

[6 pts.] A current flows in an aluminum wire with a drift speed of the conduction electrons of 0.002 m/s . The conduction electron density in aluminum is $6.0 \times 10^{28} / \text{m}^3$. What is the current density in the wire?

$3.3 \cdot 10^{24} \text{ A/m}^2$

$3.0 \cdot 10^{31} \text{ A/m}^2$

$4.3 \cdot 10^{20} \text{ A/m}^2$

$1.2 \cdot 10^{26} \text{ A/m}^2$

$1.92 \cdot 10^6 \text{ A/m}^2$

$1.92 \cdot 10^9 \text{ A/m}^2$

$J = n e v_d, v_d = 0.002 \text{ m/s}$
 $e = 1.6 \times 10^{-19} \text{ C}$

6)

[8 pts.] Calculate the power used by a circuit that has a resistance of 150Ω and draws a current of 0.4 A .

0.0026 W

0.16 W

24 W


60 W

150 W

375 W

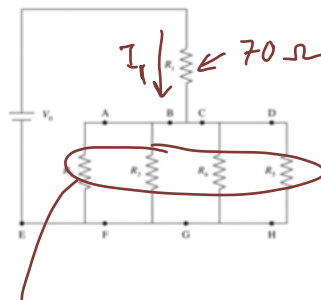7)

[10 pts.] A voltage of $V_0 = 24 \text{ V}$ is supplied to the resistor configuration shown, with $R_1 = 70 \Omega$ and $R_2=R_3=R_4=R_5 = 200 \Omega$. Calculate the current through point A (i.e., through R_2) and through point B.



$I_A = 0.15 \text{ A}$, $I_B = 0.15 \text{ A}$

$I_A = 0.15 \text{ A}$, $I_B = 0.3 \text{ A}$

$I_A = 0.05 \text{ A}$, $I_B = 0.05 \text{ A}$

$I_A = 0.05 \text{ A}$, $I_B = 0.1 \text{ A}$

$I_A = 0.02 \text{ A}$, $I_B = 0.04 \text{ A}$

$I_A = 0.01 \text{ A}$, $I_B = 0.02 \text{ A}$

$$R_{\text{eff}} = \frac{200 \Omega}{4} = 50 \Omega$$

$$\text{So } I_1 = \frac{24 \text{ V}}{(70 + 50 \Omega)} = 0.2 \text{ A},$$

thru R_1

• at center junction, junction rule & symmetry $\Rightarrow I_B = I_C = I_1/2$


$$\text{So } I_B = 0.1 \text{ A}$$

• junction at left similarly divides

I_B further in half,

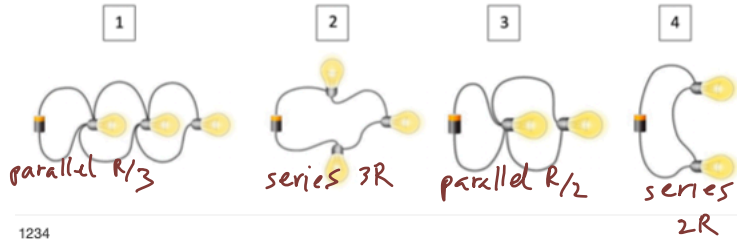8)

[8 pts.] Order the circuits shown below according to their power output, from highest to lowest. All batteries have the same voltage, and all light bulbs have the same resistance.



1234

1342

2314

2413

3412

3124

4123

4213

$$P = \frac{V^2}{R} \rightarrow \text{largest } R = \text{smallest } P$$

9)

[8 pts.] Five wires meet at a junction. In two of the wires, a current of $I_1 = 4.6 \text{ A}$ and $I_2 = 2.7 \text{ A}$ enters the junction, and in another two a current $I_3 = 2.4 \text{ A}$ and $I_4 = 5.3 \text{ A}$ exits the junction. Determine the current in wire 5.

0.2 A into the junction


0.2 A out of the junction

0.4 A into the junction

0.4 A out of the junction

0.6 A into the junction

0.6 A out of the junction

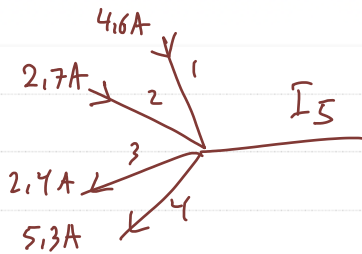


$$\sum I = 0 \text{ (junction rule)}$$

$$\text{sum of } I_1 - I_4 = 0.4 \text{ A out} \\ \rightarrow I_5 \text{ 0.4 in}$$

10)

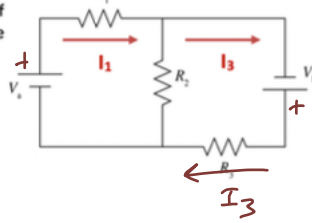10) [8 pts.] In the circuit shown $V_a = 20\text{ V}$ and $V_b = 5\text{ V}$. Which of the following relations is correct (the arrows below define the direction of current flow for I_1 and I_3).



$20\text{ V} - R_1 I_1 - 5\text{ V} + R_3 I_3 = 0$

$20\text{ V} + R_1 I_1 - 5\text{ V} - R_3 I_3 = 0$

$20\text{ V} - R_1 I_1 + 5\text{ V} + R_3 I_3 = 0$

$20\text{ V} + R_1 I_1 + 5\text{ V} - R_3 I_3 = 0$

$20\text{ V} - R_1 I_1 + 5\text{ V} - R_3 I_3 = 0$

this is loop rule for loop around perimeter

11)

11) [8 pts.] You charge an initially uncharged 68 mF capacitor through a $32\ \Omega$ resistor by means of a battery. After what time has the charge on the capacitor reached 90% of its maximum?

0.23 seconds

5 seconds

15 seconds

25 seconds

50 seconds

$$I = I_{\max} (1 - e^{-t/RC}) = 0.90$$


so $e^{-t/RC} = 0.10$ with $RC = 2.18\text{ s}$

$$t = RC \ln 10 = 5.0\text{ s}$$

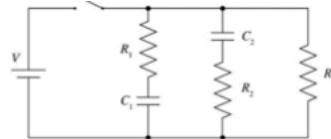12)

[5 pts.] Consider the RC circuit shown in the diagram, with a battery voltage V . Before the switch is closed, both capacitors are uncharged. All the resistances are the same and equal to R , and the capacitances are $C_2 = 2C_1$.

What is the amount of current supplied by the battery immediately after the switch is closed?



$3 \frac{V}{R}$

$\frac{V}{R}$

$\frac{2}{3} \frac{V}{R}$

$\frac{1}{2} \frac{V}{R}$

$\frac{1}{3} \frac{V}{R}$

at time = 0, capacitors have no ΔV ("like wires") so effectively the 3 resistors act as a parallel combination

$\hookrightarrow R_{\text{eff}} \Rightarrow R/3$
 so $I = \frac{\Delta V}{R_{\text{eff}}} = \frac{V}{R/3}$

13)

) [5pts] Same circuit as problem 12. What is the amount of current supplied by the battery a long time after the switch is closed?

$$\frac{3}{R} V$$

$$\frac{V}{R}$$

$$\frac{2}{3} \frac{V}{R}$$

$$\frac{1}{2} \frac{V}{R}$$

$$\frac{1}{3} \frac{V}{R}$$

0

for $t \rightarrow \infty$ capacitors don't
admit any current

Battery must supply current to
far-right resistor only,

$$R_{\text{eff}} = R.$$