

Exam-2 Phys-207 Spring '20

1) *Parallel-plate capacitor energy [8 pts.]* A parallel-plate capacitor with a non-zero charge is disconnected from any battery. If the separation of its plates is doubled, the electric energy stored in the capacitor is:

- (A) $\frac{1}{4}$ of the original
- (B) $\frac{1}{2}$ of the original
- (C) unchanged
- (D) doubled $\ll +8$
- (E) quadrupled
- (F) 8 times the original


2) *Parallel-plate capacitor with dielectric [8 pts.]* A charged air-filled capacitor is connected to a 12 V battery. A sheet of dielectric with $\kappa=5$ is inserted completely filling the volume between its plates. As a result, the electric energy stored in the capacitor is:

- (A) $\frac{1}{25}$ of the original
- (B) $\frac{1}{5}$ of the original
- (C) unchanged
- (D) 5 times the original $\ll +8$
- (E) 9 times the original
- (F) 25 times the original

3) *Capacitor electric field [8 pts.]* A fully charged parallel-plate capacitor with a plate separation of 12.5 mm and a capacitance of $10 \mu\text{F}$ stores 8 mJ of energy. Find the electric field strength inside the capacitor.

- (A) 42 V/m
- (B) 320 V/m
- (C) 1250 V/m
- (D) 2260 V/m
- (E) 3200 V/m $\ll +8$
- (F) 4200 V/m

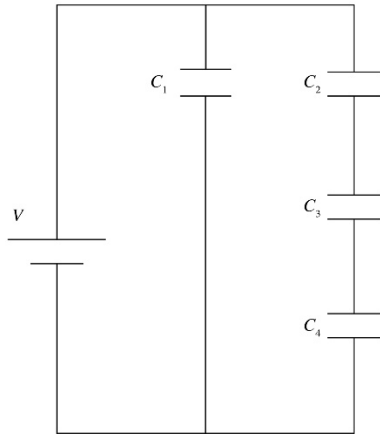4) *Capacitor circuit [10 pts.]* Consider the circuit shown with voltage V and 4 capacitors with equal capacitance C . Calculate the total capacitance and the final charge on capacitor 2, which is the top right-hand capacitor in the figure.



- (A) $C_{\text{tot}} = 1/3 \text{ C}$, $Q_2 = 1/3 \text{ CV}$
 (B) $C_{\text{tot}} = 2/3 \text{ C}$, $Q_2 = 2/3 \text{ C V}$
 (C) $C_{\text{tot}} = 3/4 \text{ C}$, $Q_2 = (3/4) \text{ (V/C)}$
 (D) $C_{\text{tot}} = 4/3 \text{ C}$, $Q_2 = 1/3 \text{ CV} \ll +10$
 (E) $C_{\text{tot}} = 4/3 \text{ C}$, $Q_2 = 2/3 \text{ V}$
 (F) $C_{\text{tot}} = 5/3 \text{ C}$, $Q_2 = 1/3 \text{ C V}$

5) *wire current density* [8 pts.] A current density of $1.6 \cdot 10^6 \text{ A/m}^2$ flows through a wire with a conduction electron density of $8.5 \cdot 10^{28} / \text{m}^3$. What is the drift speed of the electrons?

- (A) $9.4 \cdot 10^{-7} \text{ m/s}$
 (B) $4.2 \cdot 10^{-6} \text{ m/s}$
 (C) $3.3 \cdot 10^{-5} \text{ m/s}$
 (D) $1.2 \cdot 10^{-4} \text{ m/s} \ll +8$
 (E) $1.1 \cdot 10^{-3} \text{ m/s}$
 (F) $3.5 \cdot 10^{-2} \text{ m/s}$


6) *terminal voltage* [8 pts.] A battery has an EMF of 12.00 V. When you draw a current of 1.200 A from it, the terminal voltage is 10.64 V. What is terminal voltage when you draw a current of 0.600 A?

- (A) 5.30 V
 (B) 9.96 V
 (C) 10.48 V
 (D) 11.32 V $\ll +8$
 (E) 11.68 V
 (F) 11.94 V

7) *resistor network* [10 pts.] For the configuration shown below a total resistance of $R_{\text{tot}} = 2.33 \text{ R}$ is measured. The resistances $R_1 = R_2 = R_3 = R$ are also known. Determine the value of the unknown


resistance R_x .

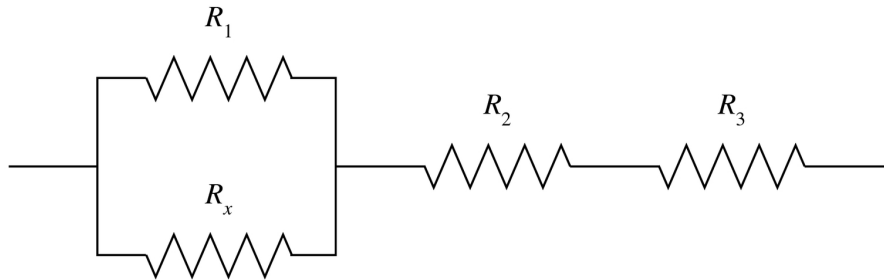- (A) $R_x = R/4$
- (B) $R_x = R/3$
- (C) $R_x = R/2 \ll +10$
- (D) $R_x = 2/3 R$
- (E) $R_x = R$
- (F) $R_x = 2R$



8) *battery-resistor network [8 pts.]* Consider the circuit shown below, with the current I_1 through R_1 going from left to right, the current I_2 through R_2 from top down and I_3 through R_3 from right to left. When applying the Kirchhoff loop rule to the left and to the right loop, respectively, one obtains:

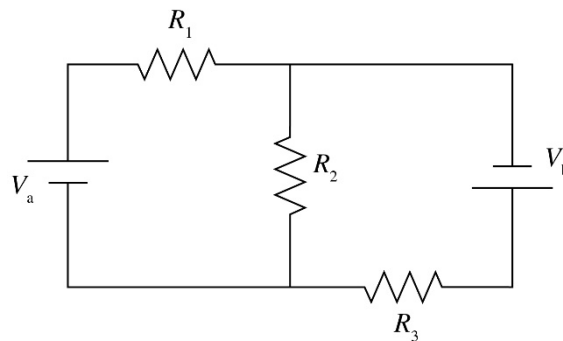- (A) $V_a - I_1 R_1 - I_2 R_2 = 0$ and $V_b - I_3 R_3 - I_2 R_2 = 0$
- (B) $V_a - I_1 R_1 - I_2 R_2 = 0$ and $V_b - I_3 R_3 + I_2 R_2 = 0 \ll +8$
- (C) $V_a + I_1 R_1 - I_2 R_2 = 0$ and $V_b - I_1 R_1 - I_2 R_2 = 0$
- (D) $V_a + I_1 R_1 - I_2 R_2 = 0$ and $V_b - I_1 R_1 - I_3 R_3 = 0$
- (E) $V_a + I_1 R_1 - I_3 R_3 = 0$ and $-V_b + I_3 R_3 + I_2 R_2 = 0$
- (F) $V_a + I_1 R_1 - I_2 R_2 = 0$ and $V_b - I_3 R_3 + I_2 R_2 = 0$




9) *lightbulb-circuits [8 pts.]* Order the circuits shown below according to their power output, from highest to lowest. All batteries have the same voltage, and all light bulbs have the same resistance.

1

2

3

4

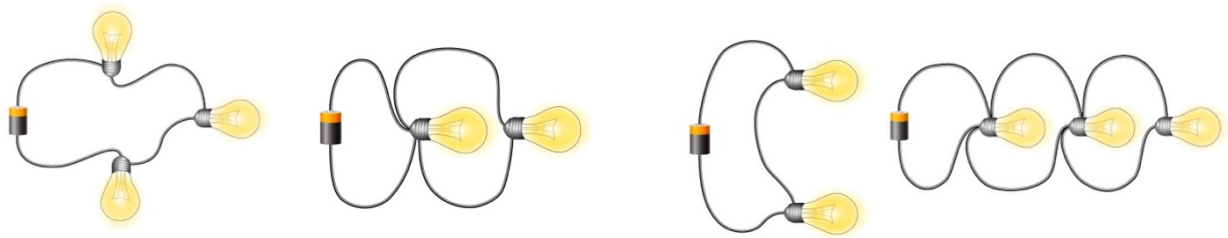

- (A) $1 > 2 > 3 > 4$
- (B) $1 > 3 > 4 > 2$
- (C) $2 > 3 > 1 > 4$
- (D) $2 > 4 > 1 > 3$
- (E) $3 > 4 > 2 > 1$
- (F) $3 > 1 > 2 > 4$
- (G) $4 > 1 > 2 > 3$
- (H) $4 > 2 > 3 > 1$ << +8

10) *appliances power [8 pts.]* A 120 V outlet is protected by a 20 A circuit breaker. Select the pair of appliances with the maximum power output that can be operated at the same time from the same outlet.

- (A) a 1150 W waffle iron and a 1300 W space heater
- (B) a 1100 W playstation and a 850 W flat iron
- (C) a 1300 W microwave and a 1000 W waffle iron
- (D) a 1500 W blow dryer and a 850 W flat-iron << +8
- (E) a 1200 W toaster and a 1050 W leaf blower
- (F) a 1300 W microwave and a 900 W waffle iron

11) *capacitor charging [8 pts.]* You charge an initially uncharged capacitor through a 400Ω resistor by means of a battery. After 0.1 s the capacitor reaches 90% of its maximum charge. What is the capacitance of the capacitor?

- (A) $109 \mu\text{F}$ << +8
- (B) $220 \mu\text{F}$
- (C) $92 \mu\text{F}$
- (D) $2200 \mu\text{F}$
- (E) $1100 \mu\text{F}$
- (F) $550 \mu\text{F}$

12) RC network [8 pts.] Consider the RC circuit shown in the diagram, with a battery voltage V . The 3 resistances are equal ($R_1 = R_2 = R_3 = R$) and the 2 capacitances are also equal ($C_1 = C_2 = C$). What is the magnitude of the current supplied by the battery a long time after the switch is closed ?

- (A) $3V/R$
- (B) $2V/R$
- (C) $V/R < +8$
- (D) $V/2R$
- (E) $V/3R$
- (F) $0 +2$

