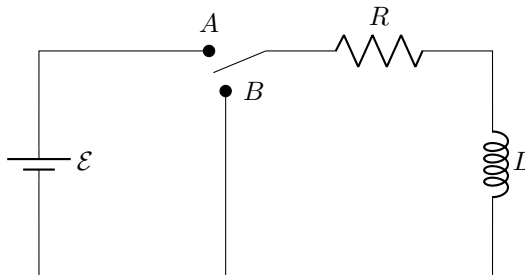


# Chapter 30 - Inductance

## Physics 207

1a. In the circuit below, suppose the switch has been in position  $A$  for a very long time. If it is then switched to  $B$ , at  $t = 0$ , find the current as a function of time. Assume all the self-inductance is contained in the coil,  $L$ .

1b. Assume the switch has been in position  $B$  for a long time. At  $t = 0$  the switch is moved to position  $A$ . At  $t_1$  the switch is moved back to  $B$ . What is the current through the resistor at  $t_2$  where  $t_2 > t_1$ ?




2. An inductor with inductance  $L$  and negligible resistance is connected to a battery, a switch  $S$ , and two resistors  $R_1$  and  $R_2$ . The battery has an emf  $\mathcal{E}$  and negligible internal resistance.  $S$  is closed at  $t = 0$ .

a) What are the currents  $i_1$ ,  $i_2$  and  $i_3$  after  $S$  has been closed a long time?

b) What are the currents  $i_1$ ,  $i_2$  and  $i_3$  after  $S$  has just been closed?

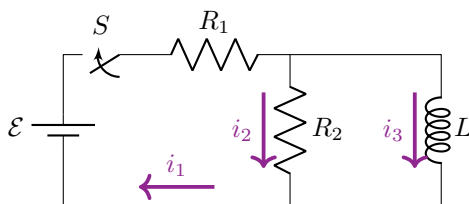
c) Apply Kirchoff's rules to the circuit and obtain a differential equation for  $i_3(t)$ . Integrate this equation to obtain an equation for  $i_3$  as a function of time  $t$  that has elapsed since  $S$  was closed.




3. a) Switch  $S_1$  is closed and switch  $S_2$  is left open. Just after  $S_1$  is closed, what are the current  $i_0$  through  $R_0$  and the potential differences  $v_{ac}$  and  $v_{bc}$ ?

b) After  $S_1$  has been closed a long time ( $S_2$  is still open) so that the current has reached its final, steady value, what are  $i_0$ ,  $v_{ac}$  and  $v_{bc}$ ?

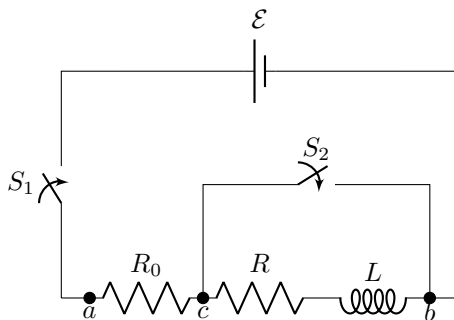c) Find the expressions for  $i_0$ ,  $v_{ac}$  and  $v_{bc}$  as functions of time  $t$  since  $S_1$  was closed.




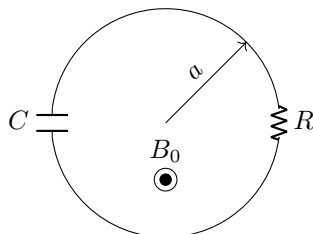4. A wire loop with radius  $a$  has a capacitor with capacitance  $C$  and a resistor with resistance  $R$  attached in series. The wire loop is placed in a uniform magnetic field,  $B_0$ , that is initially perpendicular to the loop. At  $t = 0$ , the wire loop begins to rotate with some frequency  $\omega$ . The capacitor is initially uncharged. Find the differential equation that you would use to solve for the charge on the capacitor. You do not need to solve this equation!



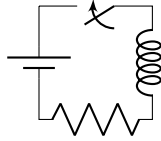5. In an RL-circuit contains a  $30.0 \Omega$  resistor, a  $12.0 \text{ V}$  battery and an unknown inductor that is in the shape of a solenoid. When the switch is closed, it takes  $24.0 \text{ ms}$  for the voltage across the inductor to drop to  $42.5\%$  of its initial value. An object that takes up the full volume of the solenoid is inserted into the inductor. When the experiment is redone, they find that it instead takes  $30.0 \text{ ms}$ .

- What are the relative permeability and magnetic susceptibility of the material the object is made of?
- Let  $B_f$  be the magnetic field in the solenoid when the object is inside and  $B_0$  without. Is  $B_f$  larger or smaller in magnitude than  $B_0$  and by what factor?
- Let  $u_f$  be the magnetic energy density in the solenoid when the object is inside and  $u_0$  without. Is  $u_f$  larger or smaller in magnitude than  $u_0$  and by what factor?



6a. In the circuit below, both switches have been open for a long time so there is no current. If switch  $S_1$  is closed at  $t = 0$ , what is the current through the  $300 \Omega$  resistor, the  $30 \text{ mH}$  and the  $50 \text{ mH}$  inductors right after the switch is closed and after the switch has been closed for a long time?

6b. Assume that  $S_2$  has been closed for a long time and  $S_1$  has been open for a long time and there is no current. Repeat part a with this new assumption.

