

# Chapter 30 - Inductance

## Physics 207

$$1a. I(t) = \frac{\mathcal{E}}{R} e^{-tR/L}$$

$$1b. I(t) = \frac{\mathcal{E}}{R} \left(1 - e^{-t_1 R/L}\right) e^{-(t_2 - t_1)R/L}$$

$$2a. i_1 = \frac{\mathcal{E}}{R_1}$$

$$i_2 = 0$$

$$i_3 = \frac{\mathcal{E}}{R_1}$$

$$2b. i_1 = \frac{\mathcal{E}}{R_1 + R_2}$$

$$i_2 = \frac{\mathcal{E}}{R_1 + R_2}$$

$$i_3 = 0$$

$$2c. i_3 = \frac{\mathcal{E}}{R_1} \left(1 - e^{\frac{-R_1 R_2 t}{L(R_1 + R_2)}}\right)$$

$$3a. i_0 = 0$$

$$v_{ac} = 0$$

$$v_{cb} = \mathcal{E}$$

$$3b. i_0 = \frac{\mathcal{E}}{R_0 + R}$$

$$v_{ac} = \frac{\mathcal{E} R_0}{R_0 + R}$$

$$v_{cb} = \frac{\mathcal{E} R}{R_0 + R}$$

$$3c. i_0(t) = \frac{\mathcal{E}}{R + R_0} \left(1 - e^{-(R+R_0)t/L}\right)$$

$$v_{ac}(t) = \frac{\mathcal{E} R_0}{R + R_0} \left(1 - e^{-(R+R_0)t/L}\right)$$

$$v_{cb}(t) = \frac{\mathcal{E} R}{R + R_0} \left(1 - e^{-(R+R_0)t/L}\right)$$

$$4. 0 = B\pi a^2 \omega \sin(\omega t) - \frac{q}{C} - \frac{dq}{dt} R$$

$$5a. K_m = 1.25$$

$$\chi_m = 0.25$$

$$5b. B_f = 1.25 B_0$$

$$5c. u_f = 1.25 u_0$$

$$6a. \text{At } t = 0: \text{ Resistor } I = 24.0 \text{ mA}$$

$$30 \text{ mH Inductor } I = 0$$

$$50 \text{ mH Inductor } I = 0$$

$$\text{At } t \rightarrow \infty: \text{ Resistor } I = 0 \text{ mA}$$

$$30 \text{ mH Inductor } I = 20.0 \text{ mA}$$

$$50 \text{ mH Inductor } I = 0$$

$$6b. \text{At } t = 0: \text{ Resistor } I = 24.0 \text{ mA}$$

$$30 \text{ mH Inductor } I = 0$$

$$50 \text{ mH Inductor } I = 0$$

$$\text{At } t \rightarrow \infty: \text{ Resistor } I = 0 \text{ mA}$$

$$30 \text{ mH Inductor } I = 0$$

$$50 \text{ mH Inductor } I = 0$$