

---

# Physics 207 – Exam 2

Sections (519-524; 525-530) – March 9, 2022


---

1) A parallel plate capacitor has capacitance  $C$  and it is charged with a charge  $Q$ . When the distance between the parallel plates is doubled, what happens to  $V$ , the potential difference between the plates, and  $U$  the potential energy of the capacitor?

- A)  $V$  becomes half as great and  $U$  becomes half as great.
- B)  $V$  becomes twice as great and  $U$  becomes half as great. [4]
- C)  $V$  becomes twice as great and  $U$  becomes twice as great. [8]
- D)  $V$  becomes half as great and  $U$  becomes four times as great.
- E)  $V$  does not change and  $U$  does not change.
- F)  $V$  becomes half as great and  $U$  becomes twice as great. [4]

2) Evaluate the equivalent capacitance of the configuration shown in Figure. All the capacitors are identical, and each has capacitance  $C$ .

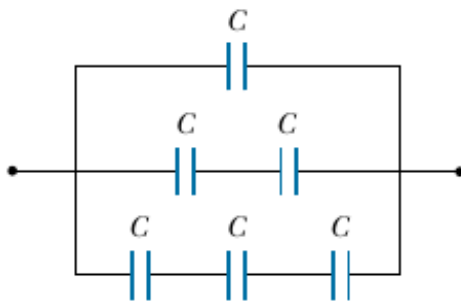- A)  $\frac{11}{6}C$  [8]
- B)  $6C$
- C)  $\frac{1}{6}C$
- D)  $\frac{13}{7}C$
- E)  $\frac{6}{11}C$  [4]
- F)  $\frac{7}{13}C$




3) You slide a slab of dielectric between the plates of a parallel-plate capacitor while keeping the *charges* on the plates constant. What happens to  $V$ , the potential difference between the two plates, and  $U$ , the potential energy of the capacitor?

- A)  $V$  decreases and  $U$  increases. [4]
- B)  $V$  increases and  $U$  decreases. [4]
- C)  $V$  decreases and  $U$  decreases. [8]
- D)  $V$  increases and  $U$  increases.
- E)  $V$  remains the same and  $U$  increase.
- F)  $V$  increases and  $U$  remains the same.

4) A  $12\mu\text{F}$  capacitor and a  $6\mu\text{F}$  capacitor are connected first in a parallel and then in a series way. If the potential difference  $V_{ab}$  is the same in both cases, what is the ratio of the charges on the  $12\mu\text{F}$  capacitor?

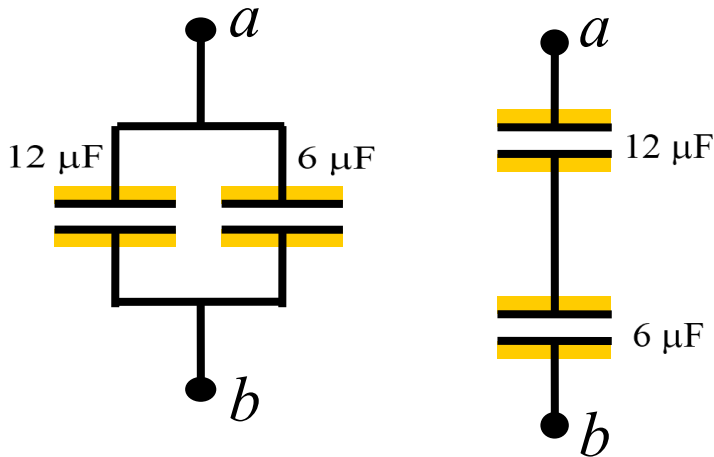- A) 3 [8]
- B) 4
- C) 5
- D)  $3/2$  [4]
- E)  $1/2$
- F) 2



5) Suppose that the current through a conductor varies with time according to the expression  $I(t) = I_0 \frac{t}{t_0}$  where  $I_0$  and  $t_0$  are constants. How much charge  $Q$  passes a fixed observation point within the conductor between  $t = 0$  and  $t = t_0$ ? If the cross-section area is  $A$ , what is the current density  $J$  at  $t = t_0$ ?


- A)  $Q = I_0 t_0/2$      $J = I_0/A$  [8]
- B)  $Q = I_0 t_0$      $J = I_0/A$  [4]
- C)  $Q = I_0 t_0/2$      $J = 2 I_0/A$  [4]
- D)  $Q = I_0$      $J = I_0$
- E)  $Q = I_0/t_0$      $J = A I_0$
- F)  $Q = I_0 t_0/3$      $J = 3 I_0/A$

6) A metal wire of resistance  $R$  is cut into three equal pieces that are then connected side by side to form a new wire whose length is equal to one-third the original length. What is the resistance of this new wire?

- A)  $3R$
- B)  $R/3$
- C)  $9R$
- D)  $R/9$  [7]
- E)  $R/2$
- F)  $R/6$


7) Consider a wire of area  $A=4 \text{ mm}^2$  and length  $l=3 \text{ m}$ . If a voltage difference of  $4.5 \text{ V}$  is applied to its ends, then a current of  $2 \text{ A}$  flows through it. Find the resistivity  $\rho$ .

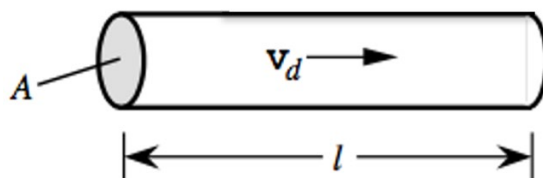- A)  $9.0 \times 10^{-9} \Omega/\text{m}$
- B)  $3.0 \times 10^6 \Omega/\text{m}$  (2)
- C)  $3.0 \times 10^{-6} \Omega\text{-m}$  (8)
- D)  $3.0 \times 10^{-3} \Omega\text{-m}$
- E)  $6.0 \times 10^{-6} \Omega/\text{m}$
- F)  $2.0 \times 10^{-9} \Omega\text{-m}$




8) The magnitudes of current following through the  $30\ \Omega$  AND  $20\ \Omega$  resistor are respectively

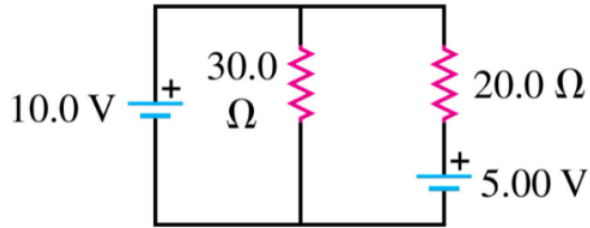- A)  $1/3\ \text{A}$ ,  $3/4\ \text{A}$  [3]
- A)  $1/3\ \text{A}$ ,  $1/4\ \text{A}$  [7]
- A)  $1/3\ \text{A}$ ,  $1/10\ \text{A}$  [2]
- A)  $1/6\ \text{A}$ ,  $3/4\ \text{A}$
- A)  $1/6\ \text{A}$ ,  $1/4\ \text{A}$  [4]
- A)  $1/6\ \text{A}$ ,  $1/10\ \text{A}$
- A)  $1/6\ \text{A}$ ,  $3/4\ \text{A}$




9) In the following circuit,  $\mathcal{E} = 12\ \text{V}$  and  $R_1 = R_2 = R_3 = R_4 = 1\ \Omega$ , the current flowing through the resistor  $R_1$  is

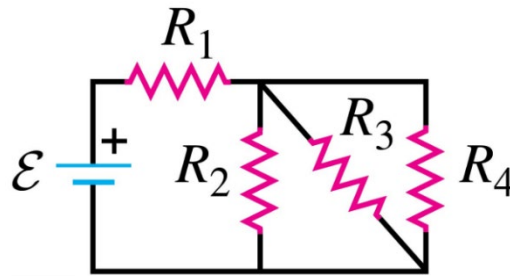- A)  $3\ \text{A}$  [2]
- B)  $4\ \text{A}$
- C)  $9\ \text{A}$  [8]
- D)  $12\ \text{A}$
- E)  $14\ \text{A}$
- F)  $16\ \text{A}$  [4]
- G)  $18\ \text{A}$  [2]




10) Three identical light bulbs are connected to a source of emf as shown. The light bulb A will shine

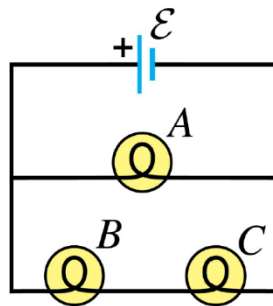- A) as bright as B
- B) as bright as C
- C) as bright as B and C combined [2]
- D) twice as bright as B [2]
- E) twice as bright as C [2]
- F) twice as bright as B and C combined [7]



11) In the following circuit, the current flowing through the  $4.00\ \Omega$  resistor is  $4.00\ \text{A}$ , the current flowing through the  $20.0\ \Omega$  resistor must be

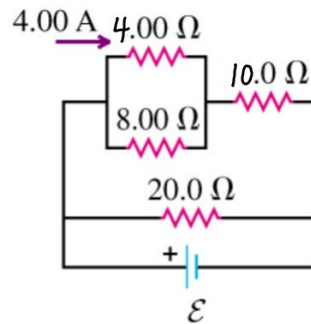- A)  $0.8\ \text{A}$  [2]
- B)  $1.2\ \text{A}$
- C)  $2.0\ \text{A}$
- D)  $3.0\ \text{A}$  [2]
- E)  $3.8\ \text{A}$  [8]
- F)  $4.6\ \text{A}$
- G)  $5.2\ \text{A}$



12) A capacitor with capacitance  $C$  is charging through a resistor  $R$  using a battery with emf  $\mathcal{E}$ . When the current is at  $1/8$  of its maximum value, the capacitor will have been charged to

- A)  $1/8$  of its maximum charge
- B)  $2/8$  of its maximum charge
- C)  $3/8$  of its maximum charge
- D)  $4/8$  of its maximum charge
- E)  $5/8$  of its maximum charge
- F)  $6/8$  of its maximum charge
- G)  $7/8$  of its maximum charge [7]

13) In the following circuit, the switch has been closed for a long time. The current through the resistor  $R_2$  and the charge on the LOWER plate of the capacitor are

- A) 2 A, 52  $\mu\text{C}$
- B) 2 A, -52  $\mu\text{C}$  [4]
- C) 3 A, 36  $\mu\text{C}$  [6]
- D) 3 A, -36  $\mu\text{C}$  [8]
- E) 4 A, 20  $\mu\text{C}$
- F) 4 A, -20  $\mu\text{C}$  [4]

